

AI UNLEASHES CHAOS

Lorenz attractor -- circuit by Paul Horowitz

PCB by Jason Gallicchio and Claude Opus 5 Max | 2026-09-15 rev A

6

$$\frac{dx}{dt} = s (y - x)$$

$$\frac{dy}{dt} = r x - y - x z$$

$$\frac{dz}{dt} = x y - b z$$

$s = 10 \quad r = 28 \quad b = 8/3$


Every term weighs 1 MEG / R: R1 = R2 = 100k is s, R3 = 35.7k is r, R7 = 374k is b.
 The MPY634s form A*B/10 and take their minus signs from swapped inputs. 0.1 V per unit; time scale tau = 1 MEG x C.

x and z on a scope in X-Y draw this





this project, and how it was made

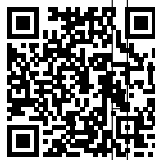

Paul's original circuit seti.harvard.edu

B

AI UNLEASHES CHAOS

Lorenz attractor -- circuit by Paul Horowitz

PCB by Jason Gallicchio and Claude Opus 5 Max | 2026-09-15 rev A

6

$$\frac{dx}{dt} = s (y - x)$$

$$\frac{dy}{dt} = r x - y - x z$$

$$\frac{dz}{dt} = x y - b z$$

$s = 10 \quad r = 28 \quad b = 8/3$

Every term weighs 1 MEG / R: R1 = R2 = 100k is s, R3 = 35.7k is r, R7 = 374k is b.
 The MPY634s form A*B/10 and take their minus signs from swapped inputs. 0.1 V per unit; time scale tau = 1 MEG x C.

x and z on a scope in X-Y draw this



this project, and how it was made



Paul's original circuit seti.harvard.edu



B

AI UNLEASHES CHAOS

Lorenz attractor



-- circuit by Paul Horowitz

PCB by Jason Galliechid and Claude Opus 5 Max

2026-09-15 rev A

$dx/dt = s (y - x)$
 $dy/dt = r x - y - x z$
 $dz/dt = x y - b z$

$s = 10$ $r = 28$ $b = 8/3$

Every term weighs 1 MEG / R: R1 = R2 = 100k is s, R3 = 35.7k is r, R7 = 374k is b.
 The MPY634s form A*B/10 and take their minus signs from swapped inputs. 0.1 V per unit; time scale tau = 1 MEG x C.

x and z on a scope in X-Y draw this



this project, and how it was made



Paul's original circuit seti.harvard.edu

AI UNLEASHES CHAOS

Lorenz attractor -- circuit by Paul Horowitz

PCB by Jason Gallicchio and Claude Opus 5 Max | 2026-09-15 rev A

6

$$\frac{dx}{dt} = s (y - x)$$

$$\frac{dy}{dt} = r x - y - x z$$

$$\frac{dz}{dt} = x y - b z$$

$s = 10 \quad r = 28 \quad b = 8/3$

Every term weighs 1 MEG / R: R1 = R2 = 100k is s, R3 = 35.7k is r, R7 = 374k is b.
 The MPY634s form A*B/10 and take their minus signs from swapped inputs. 0.1 V per unit; time scale tau = 1 MEG x C.

x and z on a scope in X-Y draw this



this project, and how it was made



Paul's original circuit seti.harvard.edu



B

AI UNLEASHES CHAOS

Lorenz attractor -- circuit by Paul Horowitz

PCB by Jason Gallicchio and Claude Opus 5 Max | 2026-09-15 rev A



x and z on a scope in X-Y draw this



this project, and how it was made

$$\frac{dx}{dt} = s(y - x)$$

$$\frac{dy}{dt} = r x - y - x z$$

$$\frac{dz}{dt} = x y - b z$$

$s = 10$ $r = 28$ $b = 8/3$

Every term weighs 1 MEG / R: R1 = R2 = 100k is s, R3 = 35.7k is r, R7 = 374k is b.
 The MPY634s form A*B/10 and take their minus signs from swapped inputs. 0.1 V per unit; time scale tau = 1 MEG x C.



Paul's original circuit seti.harvard.edu

AI UNLEASHES CHAOS

Lorenz attractor -- circuit by Paul Horowitz

PCB by Jason Gallicchio and Claude Opus 5 Max

2026-09-15 rev A

6

$$\frac{dx}{dt} = s (y - x)$$

$$\frac{dy}{dt} = r x - y - x z$$

$$\frac{dz}{dt} = x y - b z$$

$s = 10$ $r = 28$ $b = 8/3$

Every term weighs 1 MEG / R: R1 = R2 = 100k is s, R3 = 35.7k is r, R7 = 374k is b.
 The MPY634s form A*B/10 and take their minus signs from swapped inputs. 0.1 V per unit; time scale tau = 1 MEG x C.

x and z on a scope in X-Y draw this






this project, and how it was made



Paul's original circuit seti.harvard.edu

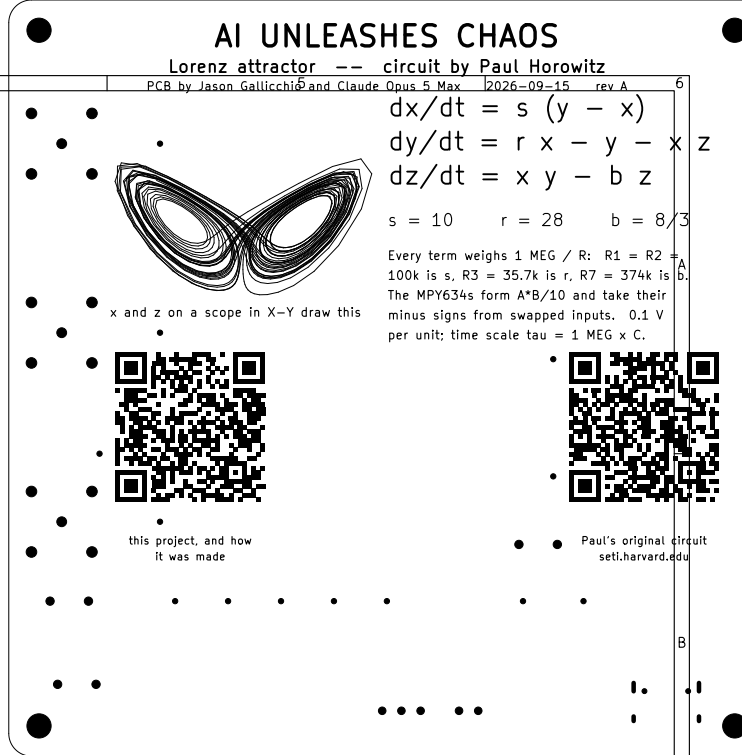

AI UNLEASHES CHAOS

Lorenz attractor -- circuit by Paul Horowitz

PCB by Jason Gallicchio and Claude Opus 5 Max | 2026-09-15 rev A

$dx/dt = s(y - x)$
 $dy/dt = r x - y - x z$
 $dz/dt = x y - b z$


$s = 10 \quad r = 28 \quad b = 8/3$

Every term weighs 1 MEG / R: R1 = R2 = 100k is s, R3 = 35.7k is r, R7 = 374k is b.
 The MPY634s form A*B/10 and take their minus signs from swapped inputs. 0.1 V per unit; time scale tau = 1 MEG x C.

x and z on a scope in X-Y draw this

this project, and how it was made

Paul's original circuit seti.harvard.edu

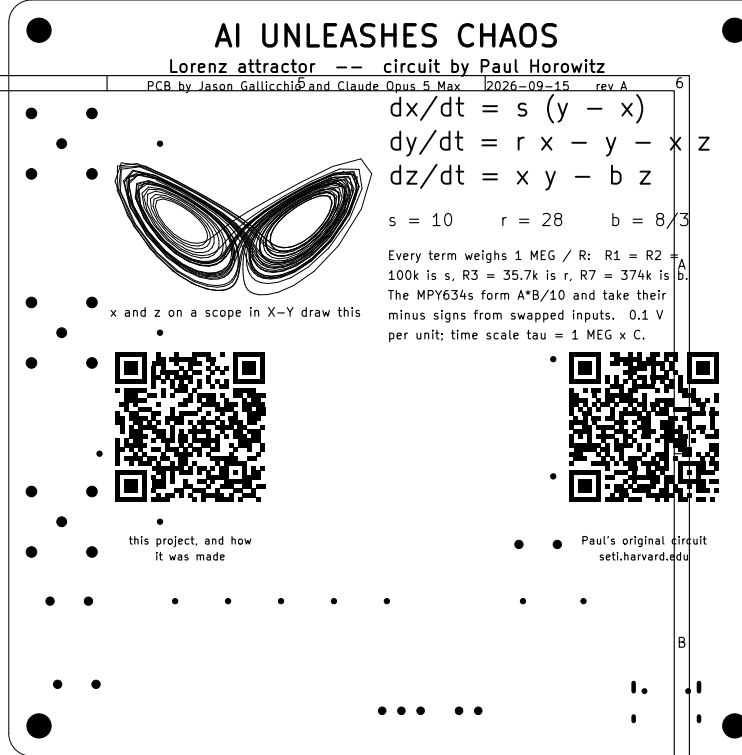

AI UNLEASHES CHAOS

Lorenz attractor -- circuit by Paul Horowitz

PCB by Jason Gallicchio and Claude Opus 5 Max | 2026-09-15 rev A

6

$$\frac{dx}{dt} = s (y - x)$$

$$\frac{dy}{dt} = r x - y - x z$$

$$\frac{dz}{dt} = x y - b z$$

$s = 10 \quad r = 28 \quad b = 8/3$


Every term weighs 1 MEG / R: R1 = R2 = 100k is s, R3 = 35.7k is r, R7 = 374k is b.
 The MPY634s form A*B/10 and take their minus signs from swapped inputs. 0.1 V per unit; time scale tau = 1 MEG x C.

x and z on a scope in X-Y draw this





this project, and how it was made

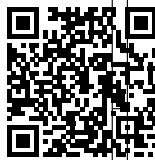

Paul's original circuit seti.harvard.edu

B

Sheet: File: lorenz.kicad_pcb		
Title:		
Size: A4	Date:	Rev:
KiCad E.D.A. 10.0.6		Id: 1/1

Sheet: File: lorenz.kicad_pcb		
Title:		
Size: A4	Date:	Rev:
KiCad E.D.A. 10.0.6		Id: 1/1

Sheet: File: lorenz.kicad_pcb		
Title:		
Size: A4	Date:	Rev:
KiCad E.D.A. 10.0.6		Id: 1/1

Sheet: File: lorenz.kicad_pcb		
Title:		
Size: A4	Date:	Rev:
KiCad E.D.A. 10.0.6		Id: 1/1